



Module: Electronics, 3rd year
**Digital Systems Design with
Hardware Description Languages**


Logic synthesis




Agenda

- **Introduction to the synthesis**
- **Synthesis of the basic elements**
- **Hardware representation of VHDL objects**
- **Synthesis of complex circuits**
- **Synthesis of types**
- **Non-synthesizable structures**

- „*A VHDL Synthesis primer*” J.Bhasker,
- „*VHDL A Logic Synthesis Approach*” D.Naylor, S.Jones,
- „*VHDL Coding and Logic Synthesis with SYNOPSIS*”
W.F.Lee,
- „*Reuse Methodology Manual*” M.Keating, P.Bricaud,
- „*Synthesis and Simulation Design Guide*” (*Xilinx manual*)
- „*Xilinx Synthesis Technology (XST) User Guide*”
(*Xilinx manual*)
- „*Digital System Design with VHDL*” M.Zwoliński
(translated: „*Projektowanie układów cyfrowych
z wykorzystaniem języka VHDL*”)

 

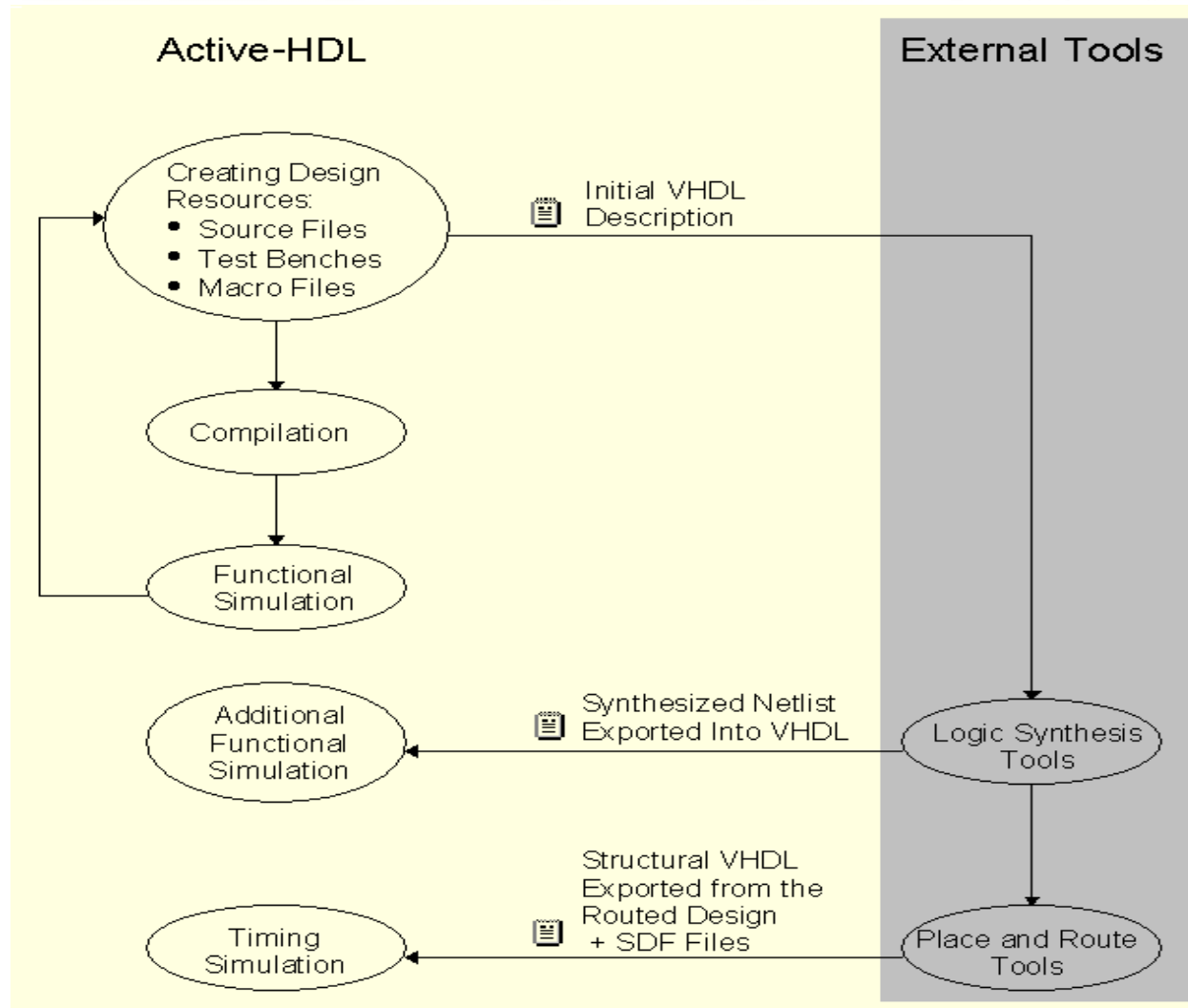Synthesis & implementation Design in Active-HDL environment




**External tools
for synthesis
and implementation**

**Graphical shell
by selecting option:**

**Tools/Preferences/
Environment/Flows/
Integrated Tools**

and

View/Flow

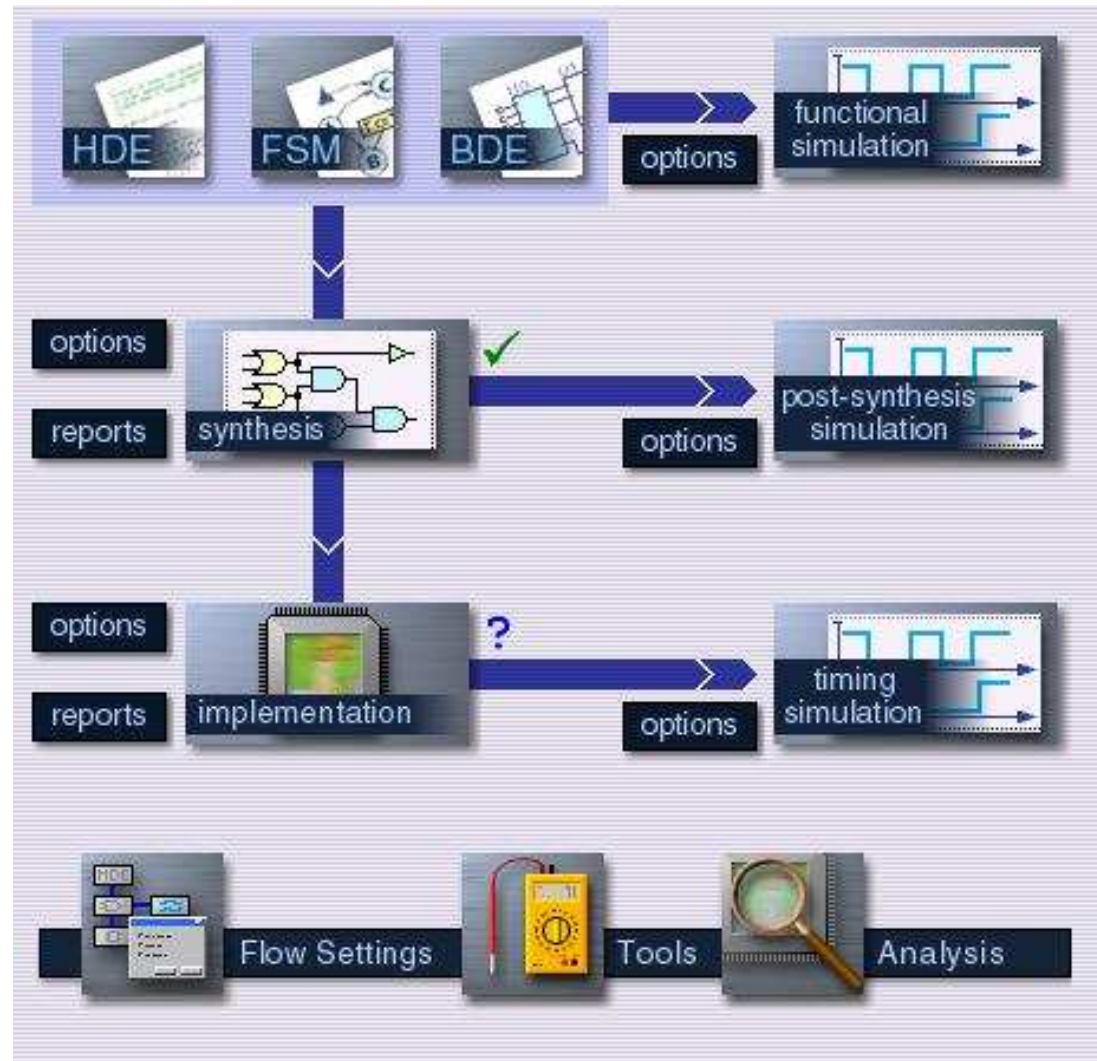


```
architecture behavioral of AND_gate is
begin
  process (A, B)                                -- synthesized AND gate
  begin
    if A = '1' and B = '1' then
      X <= '1' ;
    else
      X <= '0' ;
    end if;
  end behavioral;
```

```
architecture inferred of AND_gate is
begin                                           -- inferred AND gate
  X <= A and B;                                -- from the library of
end inferred;                                  -- presynthesized elements
```

Inferred and or xor not nor nand xnor
operators : + - * / = /= > >= < <= ...
 
```
architecture behavioral of TRI_STATE_buffer is
begin
  process (A, OE)
  begin
    if OE = '1' then
      X <= A;
    else
      X <= 'Z' ;
    end if;
  end behavioral;
```



```
architecture inferred of TRI_STATE_buffer is
begin
  X <= A when OE = '1' else 'Z' ;
end inferred;
```


Synthesis of the basic elements

Priority encoder

```

architecture concurrent of PRIORITY_encoder is
begin
code <= "0001" when sel(0) = '1' else
      "0010" when sel(1) = '1' else
      "0100" when sel(2) = '1' else
      "1000" when sel(3) = '1' else
      "0000";
end concurrent;


```

$$C_0 = S_0$$

$$C_1 = \bar{S}_0 S_1$$

$$C_2 = \bar{S}_0 \bar{S}_1 S_2$$
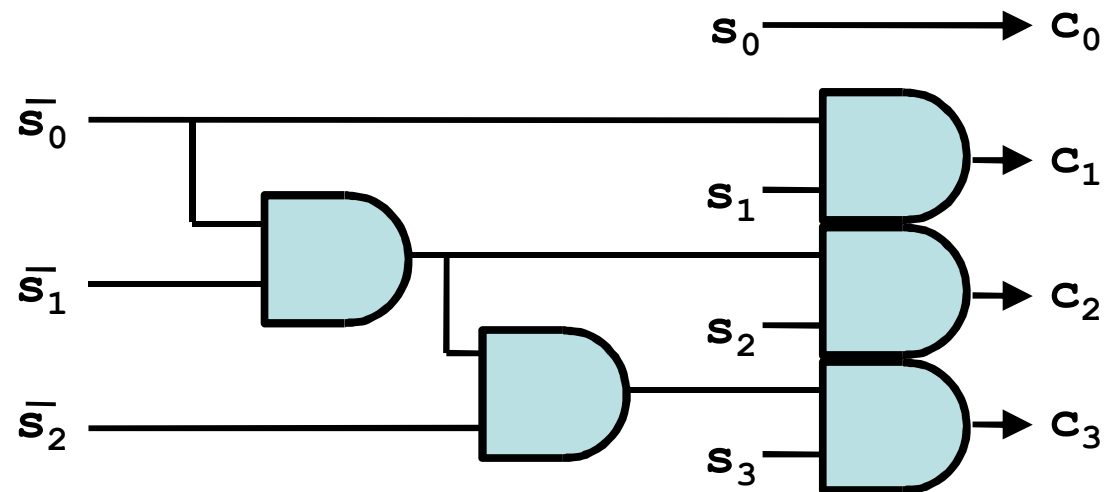
$$C_3 = \bar{S}_0 \bar{S}_1 \bar{S}_2 S_3$$



Note the logical functions implemented in LUTs!


Synthesis of the basic elements

Priority encoder

```

architecture behavioral of PRIORITY_encoder is
begin
  process (A, B, C)
  begin
    if A = '1' then           -- A: signal coming with
      X <= '1' ;             -- large delay
    elsif B = '1' then
      X <= '0' ;
    elsif C = '1' then
      X <= '1' ;
    else
      X <= '0' ;
    end if;
  end behavioral;

```

 

Note the logical functions implemented in LUTs!

An object - signal or variable - may be represented as:

- **flip-flop**
(edge-triggered memory element)
- **latch**
(level-triggered memory element)
- **wire**
(combinatorial element)



```
if C = 1 and  
    C'event  
then  
    Q <= A;  
end if;
```

signal Q:
flip-flop

```
if C = 1 then  
    Q <= A;  
else  
    -- do nothing  
end if;
```

signal Q:
latch

```
if C = 1 then  
    Q <= A;  
else  
    Q <= B;  
end if;
```

signal Q:
multiplexer



AGH

Hardware representation of objects Synthesis of D-type flip-flop

Process containing sensitivity list:

```
process (CLK)
begin
    if CLK = '1' and CLK'event then
        Q <= A and B;
    end if;
end process;
```

--rising edge

Process containing *wait* statement

```
process
begin
    wait until not CLK = '1' and CLK'event;
    Q <= A and B;
end process;
```

--falling edge

Do not combine edge detection with other conditions:

```
if CLK'event and CLK = '1' and CE = '1' then ...
```

Concurrent conditional assignment (not recommended):


```
Q <= A and B when CLK'event and CLK = '1' ;
```

Hardware representation of objects Flip-flop with Clock Enable input

```

GATECLK <= IN1 and IN2 and CLK;
process (GATECLK)
begin
  if GATECLK'event and GATECLK = '1' then
    if LOAD = '1' then
      OUT1 <= DATA;
    end if;
  end if;
end process;

```

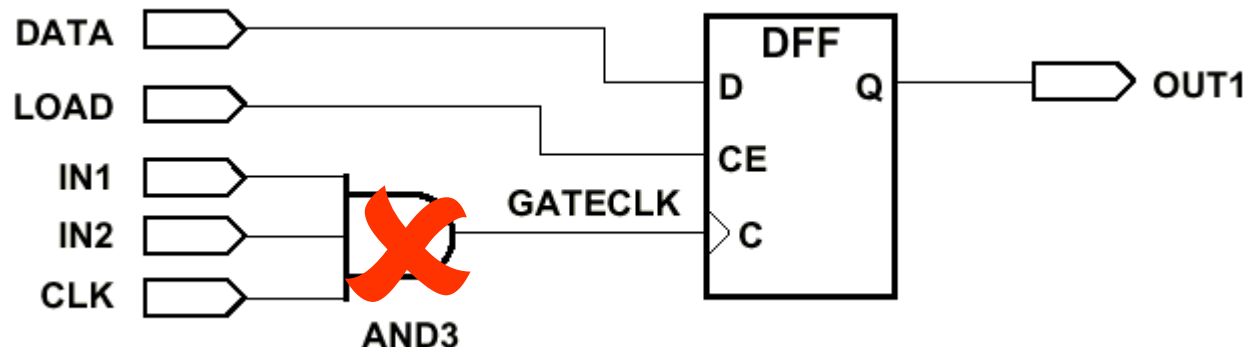


Hardware representation of objects

Flip-flop with Clock Enable input

```

ENABLE <= IN1 and IN2 and LOAD;
process (CLK)
begin
  if CLOCK'event and CLOCK = '1' then
    if ENABLE = '1' then
      OUT1 <= DATA;
    end if;
  end if;
end process;

```

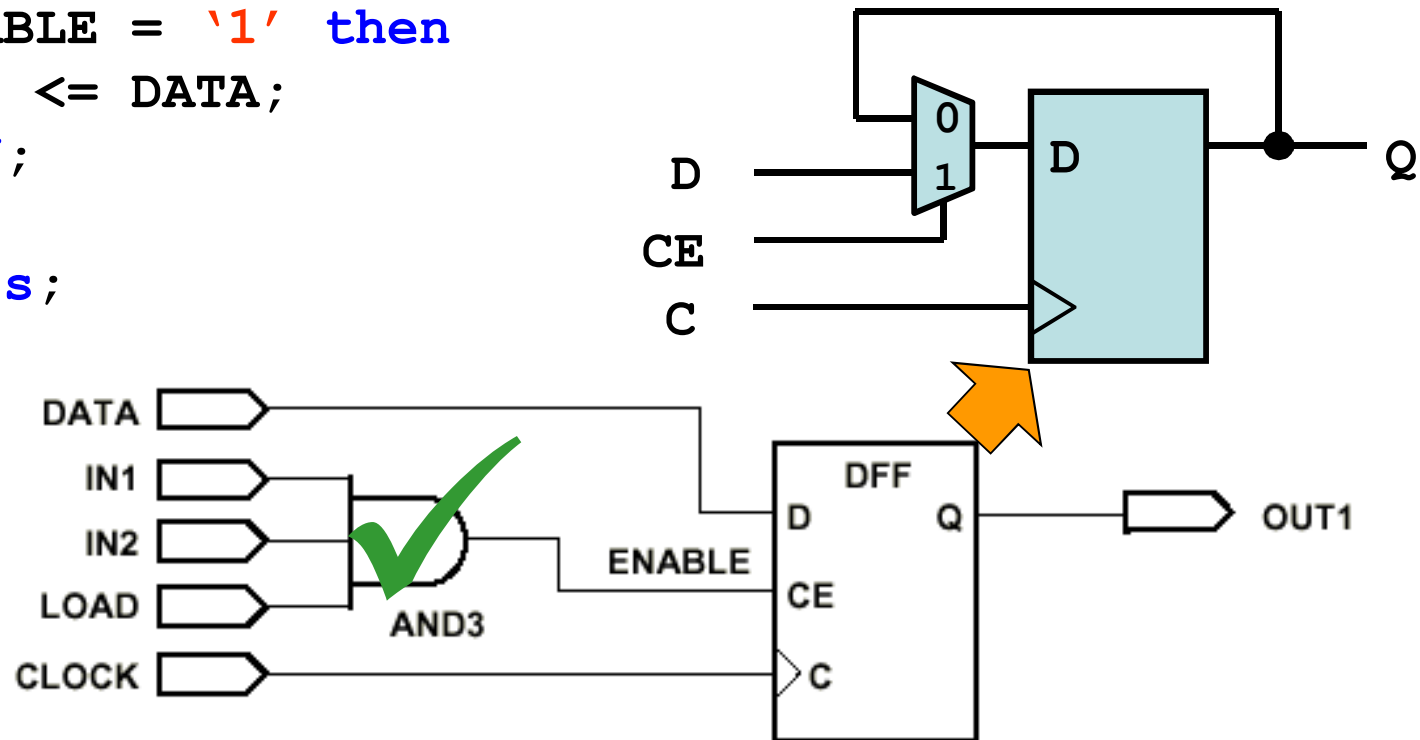

```
process (CLK)
begin
  if CLK and CLK'event then
    if SET = '1' then      -- synchronous SET
      Q <= '1';
    else
      Q <= A and B;
    end if;
  end if;
end process;

process (CLK, RESET)      -- RESET in sensitivity list!
begin
  if RESET = '1' then     -- asynchronous RESET
    Q <= '0';
  elsif CLK and CLK'event then
    Q <= A and B;
  end if;
end process;
```


Process containing sensitivity list :

```
process (CLK, A, B)           -- list of all signals...
begin                         -- ...used in the process
    if CLK = '1' then        -- active high
        Q <= A and B;
    end if;
end process;
```

Concurrent conditional assignment (not recommended):

```
Y <= A and B when CLK = '1' ;
```

```
process (A, B, C, SEL)
begin
  if SEL = "00" then
    Y <= A;
  elsif SEL = "01" then
    Y <= B;
  elsif SEL = "10" then
    Y <= C;
  end if;
end process;
```

Problem:

synthesis of latch as a result of incomplete specification of options (for **SEL = "11"** combination, the last value will be hold by default, which will imply a memory element).

```
process (A, B, C, SEL)
begin
  if SEL = "00" then
    Y <= A;
  elsif SEL = "01" then
    Y <= B;
  elsif SEL = "10" then
    Y <= C;
  elsif SEL = "11" then
    Y <= '0';
  end if;
end process;
```


Solution:

specifying all the possibilities (also in the **case** statement - here you can use the *default* specification clause **when others**).

```

signal A,B,C,D: bit
...
NO_MEMORY: process (A,B,C)
  variable TMP: bit;
begin
  TMP := A and B;
  D <= TMP or C;
end process;

```

 

Synthesis of TMP : wire

```

signal A,B,C: bit
...
IS_IT_LATCH: process (A,B,C)
  variable TMP: bit;
begin
  C <= TMP and B;
  TMP := A or C;
end process;


```

Synthesis of TMP : latch ?!

```

signal Qaux: ...
FFx2: process (clk)
begin
...
    Qaux <= D;
    Q <= Qaux;
end process;

```

 


Synthesis : 2 flip-flops

```

FFx1: process (clk)
    variable Qaux: ...
begin
...
    Qaux := D;
    Q <= Qaux;
end process;


```

 

Syntesis : 1 flip-flop


```
entity logical_ops is
  port (a, b, c, d: in bit;  m: out bit);
end logical_ops;
```
 
```
architecture example of logical_ops is
  signal e: bit;
begin
  m <= (a and b) or e;
  e <= c xor d;
end example;
```




```
entity logical_bit is
  port (a, b: in bit_vector (0 to 3);
        m: out bit_vector (0 to 3));
end logical_bit
```
 
```
architecture example of logical_bit is
begin
  m <= a and b;
end example;
```




```
entity relational_equ is
  port (a, b: in bit_vector (0 to 3);
        m: out boolean);
end relational_equ;
```
 
```
architecture example of relational_equ is
begin
  m <= a = b;
end example;
```



```
entity relational_mag is
  port (a, b: in integer range 0 to 15;
        m: out boolean);
end relational_mag;
```
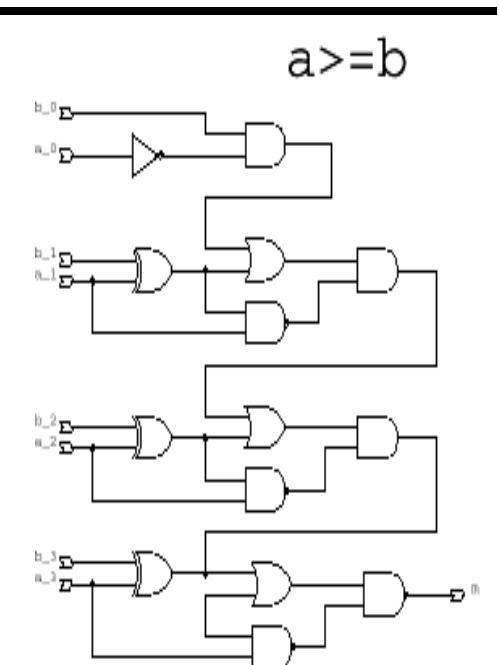
```
architecture example of relational_mag is
begin
  m <= a >= b;
end example;
```




```

package example_arithmetic is
  type small_int is range 0 to 7;
end example_arithmetic;
use work.example_arithmetic.all;

entity arith is
  port (a, b: in small_int;
        m: out small_int);
end arith;

architecture example_of_arith is
begin
  m <= a + b;
end example;

```

 


Note the hard-macros of adders (and multipliers!)

Sequential selection statements

- conditional signal assignment: `if...`
- selected signal assignment: `case...`


Concurrent selection statements

 - conditional signal assignment: `when...`
- selected signal assignment: `with...`




```
entity control_stmts is
port (a, b, c: in boolean; m: out
boolean);
end control_stmts;
```

 
```
architecture example of control_stmts
is
begin
  process (a, b, c)
    variable n: boolean;
    begin
      if a then
        n := b;
      else
        n := c;
      end if;
      m <= n;
    end process;
  end example;
```



```
entity control_stmts is
port (sel: bit_vector (0 to 1); a,b,c,d: bit;
      m: out bit);
end control_stmts;
```

```
architecture example of control_stmts is      case
begin
```
 
```
  process (sel,a,b,c,d)
  begin
    case sel is
      when b"00" => m <= c;
      when b"01" => m <= d;
      when b"10" => m <= a;
      when others => m <= b;
    end case;
  end process;
end example;
```






```
entity control_stmts is
  port (a, b, c: in boolean; m: out boolean);
end control_stmts;
architecture example of control_stmts is
begin
  m <= b when a else c;
end example;
```

```
entity control_stmts is
  port (sel: bit_vector (0 to 1); a,b,c,d: bit; m: out bit);
end control_stmts;
architecture example of control_stmts is
begin
  with sel select
    m <= c when b"00",
    m <= d when b"01",
    m <= a when b"10",
    m <= b when others;
end example;
```

```
entity loop_stmt is
port (a: bit_vector (0 to 3);
      m: out bit_vector (0 to 3));
end loop_stmt;
```
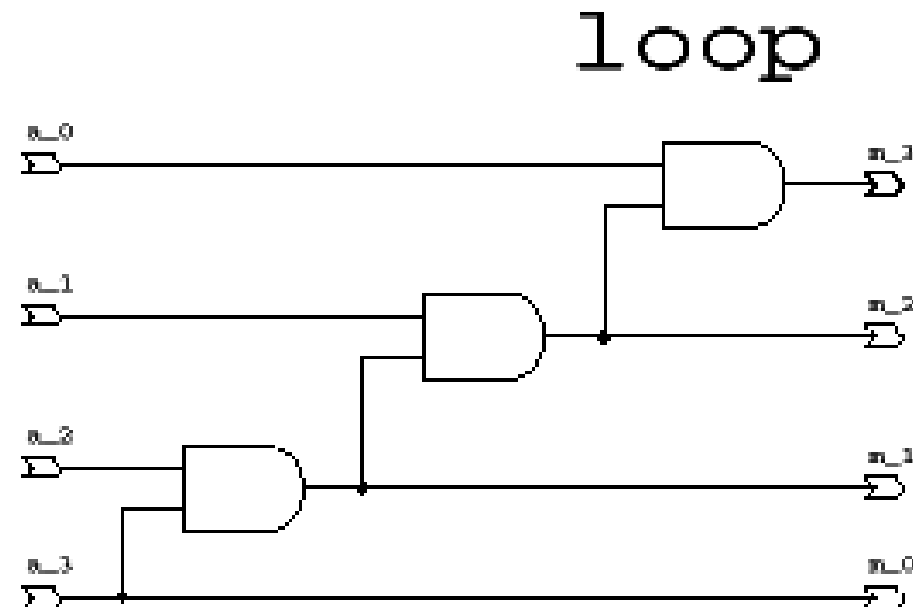
```
architecture example of loop_stmt is
begin
process (a)
  variable b: bit;
begin
  b := '1';
  for i in 0 to 3 loop
    b := a(3-i) and b;
    m(i) <= b;
  end loop;
end process;
end example;
```





AGH

Synthesis of complex circuits Logic replication - subprogram


```
entity subprograms is  
port (a: bit_vector (0 to 2);  
      m: out_bit_vector (0 to 2));  
end subprograms;
```

```
architecture example of subprograms is
```

```
function simple (w, x, y: bit) return bit is  
begin  
  return (w and x) or y;  
end;
```

```
begin  
  process (a)  
  begin  
    m(0) <= simple(a(0), a(1), a(2));  
    m(1) <= simple(a(2), a(0), a(1));  
    m(2) <= simple(a(1), a(2), a(0));  
  end process;  
end example;
```

subprogram

 

Sequential (shift register):

- with concatenation operator (&

```
shreg <= shreg (6 downto 0) & SI;
```
- with loop statement `for...loop`

```
for i in 0 to 6 loop  
    shreg(i+1) <= shreg(i);  
end loop;  
shreg(0) <= SI;
```
- with shift operators (`sll`, `srl`, ...)

Combinatorial (barrel shifter):

- with shift operators (`sll`, `srl`, ...)

```
with SEL select  
    SO <= DI when "00",  
         DI sll 1 when "01",  
         DI sll 2 when "10",  
         DI sll 3 when others;
```
- with concatenation operator (&)

Synthesis of complex circuits Memories

- inferred or instantiated
- implemented as a distributed or block memories (depending on the size, speed and occupied area)
- synchronous (optionally with asynchronous read – distributed)
- RAM (also initialized) or ROM
- also used for combinatorial logic and FSMs

Method	Advantages	Disadvantages
Inference	<ul style="list-style-type: none"> • Most generic way to incorporate RAMs into the design, allowing easy/automatic design migration from one FPGA family to another • FAST simulation 	<ul style="list-style-type: none"> • Requires specific coding styles • Not all RAMs modes are supported • Gives you the least control over implementation
CORE Generator software	Gives more control over the RAM creation	<ul style="list-style-type: none"> • May complicate design migration from one FPGA family to another • Slower simulation comparing to Inference
Instantiation	Offers the most control over the implementation	<ul style="list-style-type: none"> • Limit and complicates design migration from one FPGA family to another • Requires multiple instantiations to properly create the right RAM configuration



Synthesis of types **integer** type

- **Types and subtypes, which may represent negative values in range, are encoded in the Two's Complement code.**
- **Types and subtypes, which represent only positive values in range, are encoded in the Natural Binary Code.**
- **The number of bits used depends on the largest allowable value for the object.**

-- binary encoding having 7 bits

```
type int0 is range 0 to 100;
```

```
type int1 is range 10 to 100;
```

-- 2's complement encoding having 8 bits (including sign)

```
type int2 is range -1 to 100;
```

-- binary encoding having 3 bits

```
subtype int3 is int2 range 0 to 7;
```




Synthesis of types **integer** type

```
type short is integer 0 to 255;  
subtype shorter is short range 0 to 31;  
subtype shortest is short range 0 to 15;
```

```
signal op1, op2, res1: shortest;
```

```
signal res2: shorter;
```

```
signal res3: short;
```

```
begin
```

```
    res1 <= op1 + op2;    -- truncate carry
```

```
    res2 <= op1 + op2;    -- use carry
```

```
    res3 <= op1 + op2;    -- use carry and zero extend
```

Declaration:

```

type direction is (left, right, up, down);           -- two wires
type cpu_op is (execute, load, store);              -- two wires
                                                    -- the encoding of 11 is a "don't care"

subtype mem_op is cpu_op range load to store;       -- two wires
                                                    -- the encodings of 00 and 11 are "don't cares"

-- User Defined Encoding
attribute enum_encoding: string;
attribute enum_encoding of cpu_op: type is
    "001" &      -- execute
    "010" &      -- load
    "100";       -- store

```



... is synthesized as:

Synthesis of types

Enumerated and other types

- During synthesis the enumerated types are coded binary by default. Subsequent elements (L) of the enumerated type receive subsequent values, the first from the left receives value zero.
- Number of bits (N) of an object that represents the enumerated type will be the smallest possible number, satisfying the condition: $L \leq 2^N$
- **bit** & **boolean** types are synthesized as scalar
- **character** type is synthesized as 8-bit vector



Recommended, because:

- large number of values (9), describing most of the real states in digital systems,
- is automatically initialized to the value of 'U' – this forces a designer to initialize objects explicitly.
Do not overcome this feature by initialization of signals and variables in their declaration - circuit that cannot be initialized may be obtained after synthesis in the result of such an approach.
- easy integration with other modules - eg. `integer` type can be synthesized, but the simulation will require executing time-consuming conversion functions.
- **after synthesis and implementation there is only `std_logic` type**



Synthesis of FSMs

FSM states encoding algorithms

- *Auto*
selects the needed optimization algorithms during the synthesis process
- *One-Hot*
ensures that an individual state register is dedicated to one state. Only one flip-flop is active (hot) at any time. Very appropriate with most FPGAs where a large number of flip-flops are available. Also a good alternative to optimize speed or to reduce power.
- *Compact*
minimizes the number of state variables and flip-flops. Appropriate when optimizing area.
- *Sequential*
consists of identifying long paths and applying successive radix two codes to the states on these paths. Next state equations are minimized
- *Gray*
guarantees that only one state variable switches between two consecutive states. Appropriate for controllers exhibiting long paths without branching
- *Johnson*
much like Gray option. Shows benefits with FSM containing long paths with no branching.
- *User*
causes the synthesis tool to use the encoding defined in the source file
- *Speed1*
oriented for speed optimization. The number of bits for a state register depends on the particular FSM, but generally it is greater than the number of FSM states.



Synthesis *XST Synthesis Options*

General ISE Project Std Synthesis Adv Synthesis HDL 1 HDL 2 Xilinx Specific Include Dirs Libr < >

FSM Encoding Algorithm	Auto	
Safe Implementation	No	
Case Implementation Style	None	
<input checked="" type="checkbox"/> Resource Sharing		
FSM Style	LUT	
<input checked="" type="checkbox"/> RAM Extraction		
RAM Style	Auto	
<input checked="" type="checkbox"/> ROM Extraction		
ROM style	Auto	
<input type="checkbox"/> Automatic BRAM Packing		

FSM Encoding Algorithm dropdown menu:
Auto
One-Hot
Compact
Sequential
Gray
Johnson
User
Speed 1
None

FSM Style dropdown menu:
LUT
BRAM

RAM Style dropdown menu:
Auto
Distributed
Block

- **timing clauses:**
 - assignments (**after, transport, inertial**)
 - **wait for**
- **floating-point data types (**real**)**
- **file operations – reduced:**
 - **read:** memory initialization from file
 - **write:** debug

To be continued...

