



Logic synthesis



Agenda

- **Introduction to the synthesis**
- **Hardware representation of VHDL objects**
- **Synthesis of the basic elements**
- **Synthesis of complex circuits**
- **Synthesis of types**
- **Non-synthesizable structures**
- **Synthesis rules & guides**




Logic Synthesis Literature

- „*A VHDL Synthesis primer*” J.Bhasker,
- „*VHDL A Logic Synthesis Approach*” D.Naylor, S.Jones,
- „*VHDL Coding and Logic Synthesis with SYNOPSIS*” W.F.Lee,
- „*Reuse Methodology Manual*” M.Keating, P.Bricaud,
- „*Synthesis and Simulation Design Guide*” (Xilinx manual)
- „*Xilinx Synthesis Technology (XST) User Guide*” (Xilinx manual)
- „*Digital System Design with VHDL*” M.Zwoliński (translated: „*Projektowanie układów cyfrowych z wykorzystaniem języka VHDL*”)
- *Internet resources*




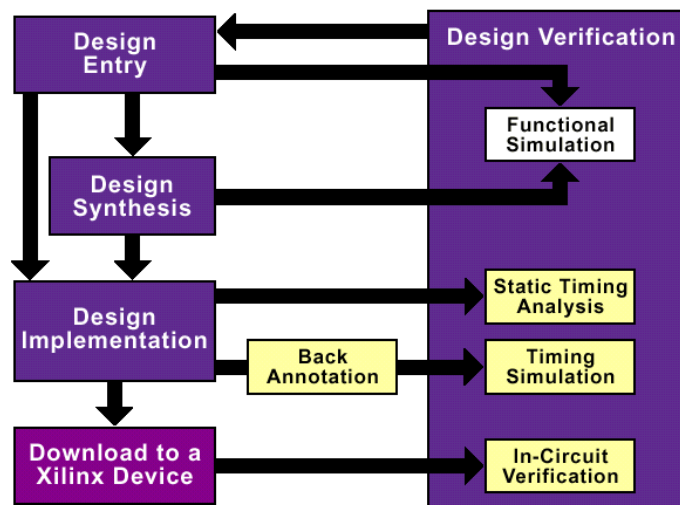Synthesis & implementation Xilinx CPLD/FPGA Design





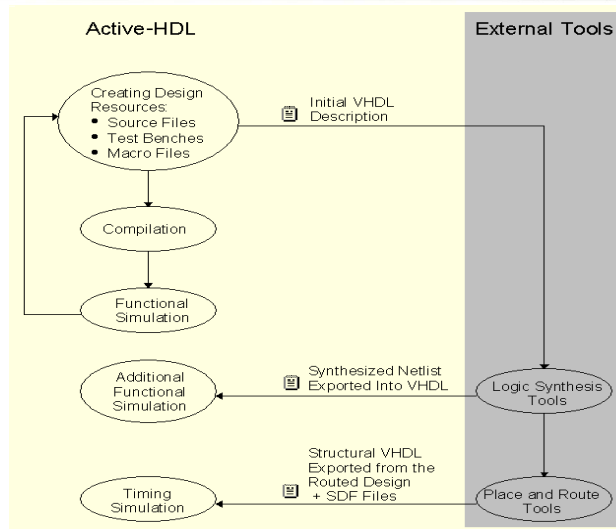Synthesis & implementation Design in Active-HDL environment



Synthesis & implementation Design in Active-HDL environment: Design Flow


External tools for synthesis and implementation


Graphical shell by selecting option:

Tools/Preferences/Environment/Flows/Integrated Tools

and

View/Flow

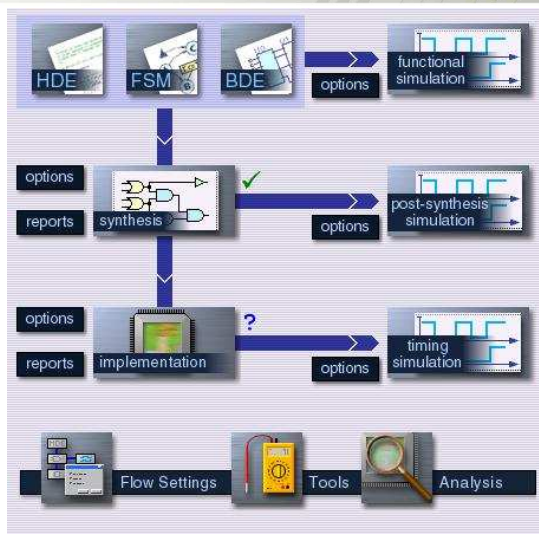

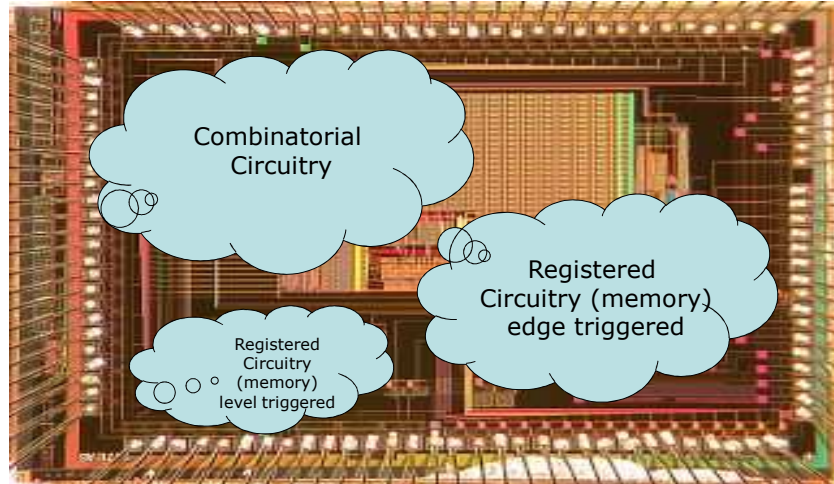

An object - signal or variable - may be represented as:

- **flip-flop**
(edge-triggered memory element)
- **latch**
(level-triggered memory element)
- **wire**
(combinatorial element)





Logic synthesis Hardware representation of VHDL objects

```
if C = '1' and
  C' event
then
  Q <= A;
end if;
```

signal Q:
flip-flop

(edge-triggered
memory element)

```
if C = '1'
then
  Q <= A;
else
  -- do nothing
end if;
```

signal Q:
latch

(level-triggered
memory element)

```
if C = '1'
then
  Q <= A;
else
  Q <= B;
end if;
```

signal Q:
multiplexer

(combinatorial
element)



Synthesis of the basic elements Arithmetic and logical operators

```
architecture behavioral of AND_gate is
begin
  process (A, B)
  begin
    if A = '1' and B = '1' then
      X <= '1';
    else
      X <= '0';
    end if;
  end behavioral;

  architecture inferred of AND_gate is
  begin
    X <= A and B;
  end inferred;
```


Inferred operators: and or xor not nor nand xnor
+ - * / = /= > >= < <= ...



Synthesis of the basic elements Tri-state buffer

AGH
 
```
architecture behavioral of TRI_STATE_buffer is
begin
  process (A, OE)
  begin
    if OE = '1' then
      X <= A;
    else
      X <= 'Z';
    end if;
  end behavioral;
end behavioral;
```



```
architecture inferred of TRI_STATE_buffer is
begin
  X <= A when OE = '1' else 'Z';
end inferred;
```



Synthesis of the basic elements Priority encoder

AGH


```
architecture concurrent of PRIORITY_encoder is
begin
  code <= "0001" when sel(0) = '1' else
         "0010" when sel(1) = '1' else
         "0100" when sel(2) = '1' else
         "1000" when sel(3) = '1' else
         "0000";
end concurrent;
```

$$C_0 = S_0$$

$$C_1 = \bar{S}_0 S_1$$

$$C_2 = \bar{S}_0 \bar{S}_1 S_2$$
 
$$C_3 = \bar{S}_0 \bar{S}_1 \bar{S}_2 S_3$$




Note the logical functions implemented in LUTs!



Synthesis of the basic elements Priority encoder

AGH
 
```
architecture behavioral of PRIORITY_encoder is
begin
  process (A, B, C)
  begin
    if A = '1' then      -- A: signal coming with
      X <= '1';         -- large delay
    elsif B = '1' then
      X <= '0';
    elsif C = '1' then
      X <= '1';
    else
      X <= '0';
    end if;
  end behavioral;
end;
```



Note the logical functions implemented in LUTs!



Hardware representation of objects Synthesis of D-type flip-flop

AGH

Process containing sensitivity list:

```
process (CLK)
begin
  if CLK = '1' and CLK'event then      --rising edge
    Q <= A and B;
  end if;
end process;
```

Process containing wait statement

```
process
begin
  wait until not CLK = '1' and CLK'event;      --falling edge
  Q <= A and B;
end process;
```

Do not combine edge detection with other conditions:

```
if CLK'event and CLK = '1' and CE = '1' then ...
```

Concurrent conditional assignment (not recommended):


```
Q <= A and B when CLK'event and CLK = '1';
```



Hardware representation of objects Flip-flop with Clock Enable input

AGH
 
```
GATECLK <= IN1 and IN2 and CLK;  
process (GATECLK)  
begin  
  if GATECLK'event and GATECLK = '1' then  
    if LOAD = '1' then  
      OUT1 <= DATA;  
    end if;  
  end if;  
end process;
```



Rajda & Kasperek © 2017 Dept. of Electronics, AGH UST


15



Hardware representation of objects Flip-flop with Clock Enable input

AGH
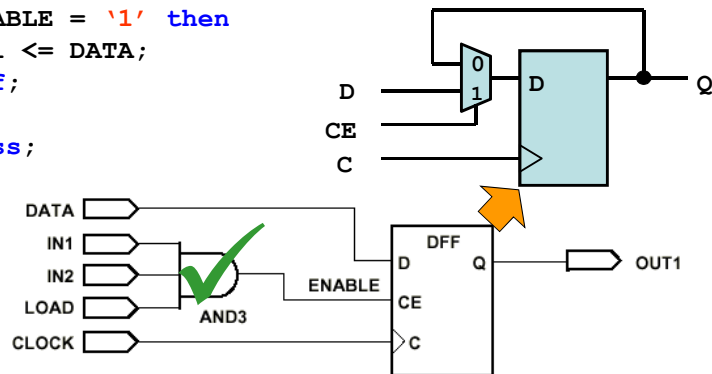
```
ENABLE <= IN1 and IN2 and LOAD;  
process (CLK)  
begin  
  if CLOCK'event and CLOCK = '1' then  
    if ENABLE = '1' then  
      OUT1 <= DATA;  
    end if;  
  end if;  
end process;
```



Rajda & Kasperek © 2017 Dept. of Electronics, AGH UST

16



Hardware representation of objects Synthesis of Set / Reset inputs

AGH

```
process (CLK)
begin
  if CLK and CLK'event then
    if SET = '1' then      -- synchronous SET
      Q <= '1';
    else
      Q <= A and B;
    end if;
  end if;
end process;

process (CLK, RESET)      -- RESET in sensitivity list!
begin
  if RESET = '1' then    -- asynchronous RESET
    Q <= '0';
  elsif CLK and CLK'event then
    Q <= A and B;
  end if;
end process;
```



Hardware representation of objects Synthesis of D-type latch

AGH

Process containing sensitivity list :

```
process (CLK, A, B)      -- list of all signals...
begin                  -- ...used in the process
  if CLK = '1' then    -- active high
    Q <= A and B;
  end if;
end process;
```

Concurrent conditional assignment (not recommended):

```
Y <= A and B when CLK = '1';
```



Hardware representation of objects Unintentional synthesis of latch

AGH

```
process (A, B, C, SEL)
begin
  if SEL = "00" then
    Y <= A;
  elsif SEL = "01" then
    Y <= B;
  elsif SEL = "10" then
    Y <= C;
  end if;
end process;
```

Problem:

synthesis of latch as a result of incomplete specification of options (for SEL = "11" combination, the last value will be hold by default, which will imply a memory element).

```
process (A, B, C, SEL)
begin
  if SEL = "00" then
    Y <= A;
  elsif SEL = "01" then
    Y <= B;
  elsif SEL = "10" then
    Y <= C;
  elsif SEL = "11" then
    Y <= '0';
  end if;
end process;
```

Solution:


specifying all the possibilities (also in the case statement - here you can use the *default* specification clause **when others**).



Hardware representation of objects Signals and variables

AGH
 
```
signal A,B,C,D: bit
...
NO_MEMORY: process (A,B,C)
  variable TMP: bit;
begin
  TMP := A and B;
  D <= TMP or C;
end process;
```



Synthesis of TMP : wire

```
signal A,B,C: bit
...
IS_IT_LATCH: process (A,B,C)
  variable TMP: bit;
begin
  C <= TMP and B;
  TMP := A or C;
end process;
```

Synthesis of TMP : latch ?!




Hardware representation of objects Signals and variables

AGH

```

signal Qaux: ...
FFx2: process (clk)
begin
...
Qaux <= D;
Q <= Qaux;
end process;

```

 


Synthesis : 2 flip-flops

```

FFx1: process (clk)
variable Qaux: ...
begin
...
Qaux := D;
Q <= Qaux;
end process;

```

 

Synthesis : 1 flip-flop

Rajda & Kasperek © 2017 Dept. of Electronics, AGH UST

21



Synthesis of complex circuits Logical operators

AGH

```


entity logical_ops is
port (a, b, c, d: in bit; m: out bit);
end logical_ops;

```

```

architecture example of logical_ops is
signal e: bit;
begin
m <= (a and b) or e;
e <= c xor d;
end example;

```

 

```


entity logical_bit is
port (a, b: in bit_vector (0 to 3);
m: out bit_vector (0 to 3));
end logical_bit

```

```

architecture example of logical_bit is
begin
m <= a and b;
end example;

```

 

Rajda & Kasperek © 2017 Dept. of Electronics, AGH UST

22




Synthesis of complex circuits Relational operators

AGH


```
entity relational_equ is
  port (a, b: in bit_vector (0 to 3);
        m: out boolean);
end relational_equ;

 architecture example of relational_equ is
begin
  m <= a = b;
end example;
```



```
entity relational_mag is
  port (a, b: in integer range 0 to 15;
        m: out boolean);
end relational_mag;

 architecture example of relational_mag is
begin
  m <= a >= b;
end example;
```



Rajda & Kasperek © 2017 Dept. of Electronics, AGH UST

23




Synthesis of complex circuits Arithmetic operators

AGH

```
package example_arithmetic is
  type small_int is range 0 to 7;
end example_arithmetic;
use work.example_arithmetic.all;

entity arith is
  port (a, b: in small_int;
        m: out small_int);
end arith;

 architecture example of arith is
begin
  m <= a + b;
end example;
```



Note the hard-macros of adders (and multipliers!)

Rajda & Kasperek © 2017 Dept. of Electronics, AGH UST

24



Synthesis of complex circuits Selection statements


AGH

Sequential selection statements

- conditional signal assignment: `if...`
- selected signal assignment: `case...`

Concurrent selection statements

 - conditional signal assignment: `when...`
- selected signal assignment: `with...`




Synthesis of complex circuits Sequential selection statements: `if`

AGH

```
entity control_stmts is
port (a, b, c: in boolean; m: out
boolean);
end control_stmts;
```
 
```
architecture example of control_stmts
is
begin
  process (a, b, c)
    variable n: boolean;
    begin
      if a then
        n := b;
      else
        n := c;
      end if;
      m <= n;
    end process;
end example;
```






AGH

```
entity control_stmts is
port (sel: bit_vector (0 to 1); a,b,c,d: bit;
      m: out bit);
end control_stmts;
```

```
architecture example of control_stmts is case
begin
```
 
```
  process (sel,a,b,c,d)
  begin
    case sel is
      when b"00" => m <= c;
      when b"01" => m <= d;
      when b"10" => m <= a;
      when others => m <= b;
    end case;
  end process;
end example;
```



AGH

```
entity control_stmts is
port (a, b, c: in boolean; m: out boolean);
end control_stmts;
architecture example of control_stmts is
begin
  m <= b when a else c;
end example;
```

```
entity control_stmts is
port (sel: bit_vector (0 to 1); a,b,c,d: bit; m: out bit);
end control_stmts;
architecture example of control_stmts is
begin
  with sel select
    m <= c when b"00",
    m <= d when b"01",
    m <= a when b"10",
    m <= b when others;
end example;
```




Synthesis of complex circuits Logic replication – loop

AGH

```
entity loop_stmt is
port (a: bit_vector (0 to 3);
      m: out bit_vector (0 to 3));
end loop_stmt;

 architecture example of loop_stmt is
begin
process (a)
variable b: bit;
begin
b := '1';
for i in 0 to 3 loop
b := a(3-i) and b;
m(i) <= b;
end loop;
end process;
end example;
```



Rajda & Kasperek © 2017 Dept. of Electronics, AGH UST

29



Synthesis of complex circuits Logic replication - subprogram

AGH


```
entity subprograms is
port (a: bit_vector (0 to 2);
      m: out bit_vector (0 to 2));
end subprograms;

architecture example of subprograms is

function simple (w, x, y: bit) return bit is
begin
return (w and x) or y;
end;

begin
process (a)
begin
m(0) <= simple(a(0), a(1), a(2));
m(1) <= simple(a(2), a(0), a(1));
m(2) <= simple(a(1), a(2), a(0));
end process;
end example;
```

subprogram

 

Rajda & Kasperek © 2017 Dept. of Electronics, AGH UST

30



Synthesis of complex circuits Shifters

Sequential (shift register):

- with concatenation operator (&)
shreg <= shreg (6 downto 0) & SI;
- with loop statemnet for...loop
for i in 0 to 6 loop
shreg(i+1) <= shreg(i);
end loop;
shreg(0) <= SI;
- with shift operators (sll, srl, ...)

Combinatorial (barrel shifter):

- with shift operators (sll, srl, ...)
with SEL select
SO <= DI when "00",
DI sll 1 when "01",
DI sll 2 when "10",
DI sll 3 when others;
- with concatenation operator (&)



Synthesis of complex circuits Memories

- inferred or instantiated
- implemented as a distributed or block memories
(depending on the size, speed and occupied area)
- synchronous (optionally with asynchronous read – distributed)
- RAM (also initialized) or ROM
- also used for combinatorial logic and FSMs

Method	Advantages	Disadvantages
Inference	<ul style="list-style-type: none"> • Most generic way to incorporate RAMs into the design, allowing easy/automatic design migration from one FPGA family to another • FAST simulation 	<ul style="list-style-type: none"> • Requires specific coding styles • Not all RAMs modes are supported • Gives you the least control over implementation
CORE Generator software	Gives more control over the RAM creation	<ul style="list-style-type: none"> • May complicate design migration from one FPGA family to another • Slower simulation comparing to Inference
Instantiation	Offers the most control over the implementation	<ul style="list-style-type: none"> • Limit and complicates design migration from one FPGA family to another • Requires multiple instantiations to properly create the right RAM configuration



Synthesis of types integer type

- Types and subtypes, which may represent negative values in range, are encoded in the Two's Complement code.
- Types and subtypes, which represent only positive values in range, are encoded in the Natural Binary Code.
- The number of bits used depends on the largest allowable value for the object.

```
-- binary encoding having 7 bits
type int0 is range 0 to 100;
type int1 is range 10 to 100;

-- 2's complement encoding having 8 bits (including sign)
type int2 is range -1 to 100;

-- binary encoding having 3 bits
subtype int3 is int2 range 0 to 7;
```



Synthesis of types integer type

```
type short is integer 0 to 255;
subtype shorter is short range 0 to 31;
subtype shortest is short range 0 to 15;

signal op1, op2, res1: shortest;
signal res2: shorter;
signal res3: short;
begin
  res1 <= op1 + op2; -- truncate carry
  res2 <= op1 + op2; -- use carry
  res3 <= op1 + op2; -- use carry and zero extend
```



Synthesis of types Enumerated types

Declaration:

```
type direction is (left, right, up, down);      -- two wires
type cpu_op is (execute, load, store);          -- two wires
                                                -- the encoding of 11 is a "don't care"

subtype mem_op is cpu_op range load to store;    -- two wires
                                                -- the encodings of 00 and 11 are "don't cares"

-- User Defined Encoding
attribute enum_encoding: string;
attribute enum_encoding of cpu_op: type is
  "001" &    -- execute
  "010" &    -- load
  "100";    -- store
```

... is synthesized as:



Synthesis of types Enumerated and other types

- During synthesis the enumerated types are coded binary by default. Subsequent elements (L) of the enumerated type receive subsequent values, the first from the left receives value zero.
- Number of bits (N) of an object that represents the enumerated type will be the smallest possible number, satisfying the condition: $L \leq 2^N$
- **bit** & **boolean** types are synthesized as scalar
- **character** type is synthesized as 8-bit vector



Synthesis of types `std_logic_1164` type

AGH

Recommended, because:

- large number of values ('U','1','0','Z','H','L','W','-','X'), describing most of the real states in digital systems,
- is automatically initialized to the value of 'U' – this forces a designer to initialize objects explicitly.
Do not overcome this feature by initialization of signals and variables in their declaration - circuit that cannot be initialized may be obtained after synthesis in the result of such an approach.
- easy integration with other modules - eg. `integer` type can be synthesized, but the simulation will require executing time-consuming conversion functions.
- **after synthesis and implementation there is only `std_logic` type**



Synthesis of FSMs FSM states encoding algorithms

AGH

- *Auto*
selects the needed optimization algorithms during the synthesis process
- *One-Hot*
ensures that an individual state register is dedicated to one state. Only one flip-flop is active (hot) at any time. Very appropriate with most FPGAs where a large number of flip-flops are available. Also a good alternative to optimize speed or to reduce power.
- *Compact*
minimizes the number of state variables and flip-flops. Appropriate when optimizing area.
- *Sequential*
consists of identifying long paths and applying successive radix two codes to the states on these paths. Next state equations are minimized
- *Gray*
guarantees that only one state variable switches between two consecutive states. Appropriate for controllers exhibiting long paths without branching
- *Johnson*
much like Gray option. Shows benefits with FSM containing long paths with no branching.
- *User*
causes the synthesis tool to use the encoding defined in the source file
- *Speed1*
oriented for speed optimization. The number of bits for a state register depends on the particular FSM, but generally it is greater than the number of FSM states.



Synthesis XST Synthesis Options

The screenshot shows the XST Synthesis Options dialog box. The tabs are: General, ISE Project, Std Synthesis, Adv Synthesis, HDL 1, HDL 2, Xilinx Specific, Include Dirs, and Libr. The options are:

- FSM Encoding Algorithm: Auto (dropdown menu open showing: Auto, One-Hot, Compact, Sequential, Gray, Johnson, User, Speed1, None)
- Safe Implementation: No
- Case Implementation Style: None
- Resource Sharing:
- FSM Style: LUT (dropdown menu open showing: LUT, BRAM)
- RAM Extraction:
- RAM Style: Auto (dropdown menu open showing: Auto, Distributed, Block)
- ROM Extraction:
- ROM style: Auto (dropdown menu open showing: Auto, Distributed, Block)
- Automatic BRAM Packing:

Green arrows point to the dropdown menus for FSM Encoding Algorithm, FSM Style, RAM Style, and ROM style.



Synthesis Non-synthesizable structures

- **timing clauses:**
 - assignments (**after**, **transport**, **inertial**)
 - **wait for**
- **floating-point data types** (**real**)
- **file operations – reduced:**
 - **read:** memory initialization from file
 - **write:** debug



Synthesis ready coding

AGH

1. Only one attribute signal 'event' in the process (clk!)
2. Drive every signal from exactly one process or use the concurrent assignment.
3. Use std_logic (and std_logic_vector) types.
4. Do not test signal/variables for 'X' or 'Z'.
5. Use asynchronous reset when there is one global signal from outside – do not generate your own asynchronous reset – use the synchronous one.
6. Highly recommended fully synchronous design
 - One global clock. Do not generate clock signals. Use multiplexers to create "load enable" signals on flip-flops. Avoid clock gating.
 - Flip-flops generate inputs to combinational logic, which computes inputs to flip-flops
 - Exactly one value per signal per clock cycle
 - Edge-triggered flip-flops only. Do not use level-sensitive logic.
 - Output registers for signals


Rajda & Kasperek © 2017 Katedra Elektroniki AGH

41



Synthesis ready coding

AGH

 

Synchronous project:

- one global CLK
- all flip-flops active on the same clock edge


Problems with two clock edges :

- *duty cycle* vulnerability
- JTAG 1149 testing

Rajda & Kasperek © 2017 Katedra Elektroniki AGH



Synthesis ready coding

 


Asynchronous clock – problems!
(worse timing, testing troubles, phase vulnerability)


Solution – CE input –
if ce='1' after (new line!) if clk'event and clk='1'.



Synthesis ready coding

 


Do not use internally generated clocks

 

Synchronous design with CE (and/or DLL modules).



Synthesis ready coding

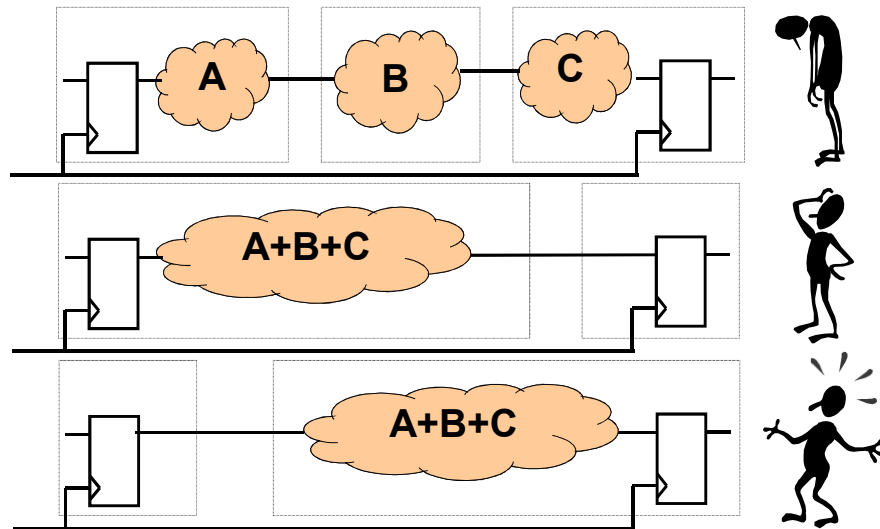

Rajda & Kasperek © 2017 Katedra Elektroniki AGH



Synthesis guides – there are many of them... AHDL language assistant

Language Assistant

VHDL

- Synthesis templates
 - Adders
 - Accumulator
 - Adder with carry in
 - Adder with carry out
 - Simple adder/subtractor
 - Comparators
 - Equality comparator
 - 'Greater-than' comparator
 - 'Less-than' comparator
 - 'Not-greater-than' comparator
 - 'Not-less-than' comparator
 - Unequality comparator
 - Counters
 - Asynchronous binary counter
 - Prescaler
 - Synchronous binary counter (for INTEG)
 - Synchronous binary counter (for STD_LO)
 - Synchronous gray counter (for STD_LO)
 - Decoders

```
--Synchronous binary up/down counter (for INTEGERS)
--CLK: in STD LOGIC;
--RESET: in STD LOGIC;
--CE, LOAD, DIR: in STD LOGIC;
--DIN: in INTEGER range 0 to 2**WIDTH-1;
--COUNT: out INTEGER range 0 to 2**WIDTH-1;

-- The declaration of the auxiliary signal 'COUNTER' must be inserted in
-- the architecture declarative part:
-- signal COUNTER: INTEGER range 0 to 2**WIDTH-1;

process (CLK, RESET)
begin
  if RESET='1' then
    COUNTER <= 0;
  elsif CLK='1' and CLK'event then
    if LOAD='1' then
      COUNTER <= DIN;
    else
      if CE='1' then
        if DIR='1' then
          if COUNTER = 15 then
            COUNTER <= 0;
          else

```

Rajda & Kasperek © 2017 Katedra Elektroniki AGH

46

To be continued...

